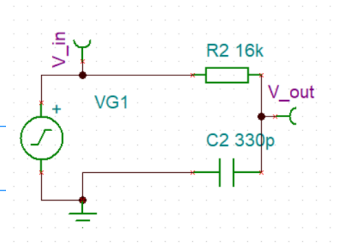



RC trece jos



Semnal sinusoidal


$f = 4\text{kHz}$

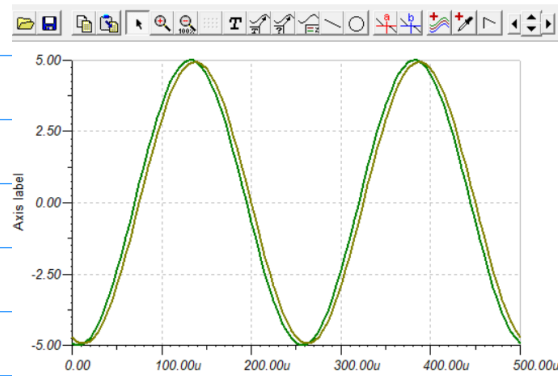Setari VG1: DC level = 5, Signal = Sine wave
Setari Sine wave: A = 5, $f = 4\text{k}$, faza = 0




VP_V_in	5V / -90°
VP_V_out	4.96V / -97.56°

$f = 40\text{kHz}$

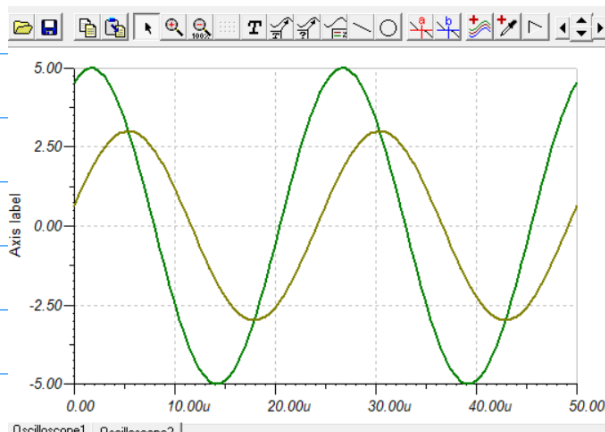


VP_V_in	5V / -90°
VP_V_out	3.01V / -143°

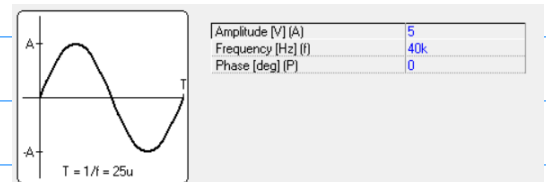Similar si la celelalte, modific doar frecventa



$f = 400\text{kHz}$

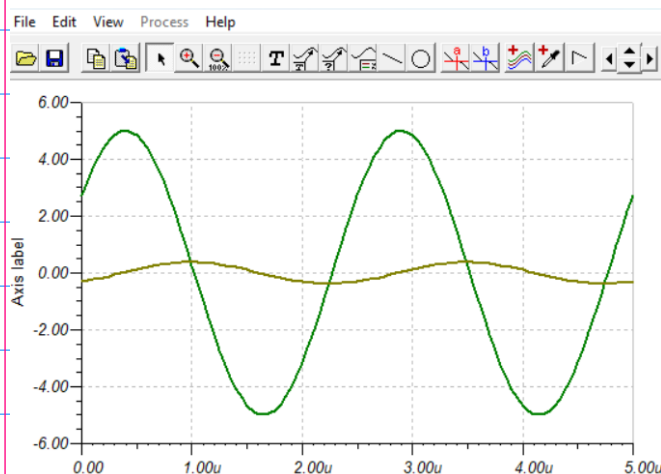


VP_V_in	5V / -90°
VP_V_out	375.72mV / -175.69°

Semnal rectangular


→ Signal : Square Wave, in rest acelasi procedeu

$f = 4\text{kHz}$

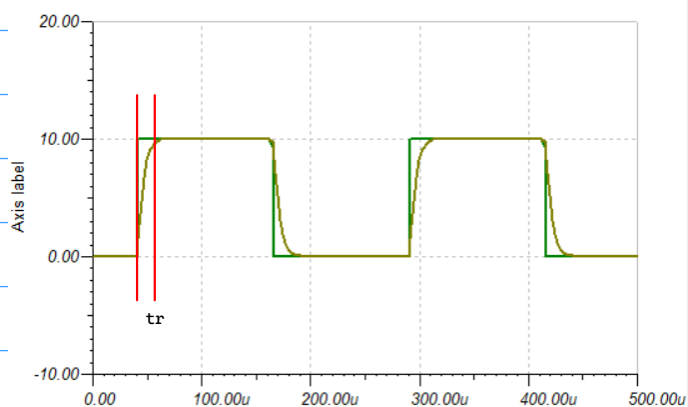


$tr = 25.22u$

$f = 40\text{kHz}$

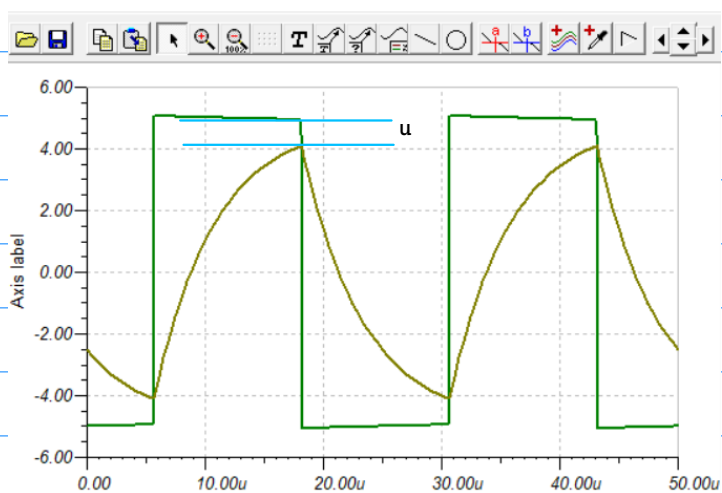

$u \sim 0.9V$

$f = 400\text{kHz}$

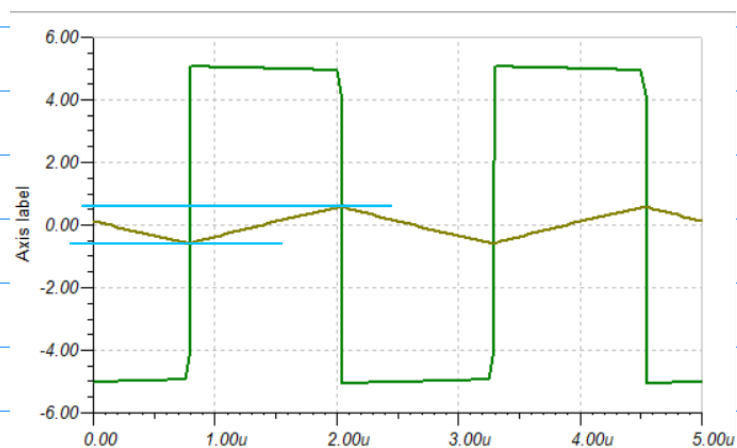

$u \sim 1,1V$